

Continuous-Time DS Modulators for RF Applications

April 14 2005


Joe Jensen

Todd Kaplan


HRL Laboratories, LLC

ADCs in Digital Receivers: Towards the “Software Radio”


Conventional Receiver

 

Digital IF Receiver

 

Digital RF Receiver

 

Trend - Eliminate Downconversion

Advantages:


- Digital robustness
- frequency agility
- Lower I/Q Images
- Better Channel Match
- Flexibility with communication standards
- More Deg of Freedom

Challenges:

- ADC needs enormous dynamic range
- Enormous data reduction needed in DSP

Issues in Moving ADC forward in Signal Path in Digital Receivers

- **High ADC sample rates required**
 - High input bandwidth and fast settling needed for sub-sampling approaches
 - Direct sampling requires higher sample rate than the IF or RF being sampled
- **High ADC dynamic range required**
 - Interfering signals in digital receiver are blocked after the ADC
 - Additional ADC dynamic range is need to replace blocking filters and AGC functions
- **ADC limitations**
 - Increasing the sample rate of ADCs decreases the ADC dynamic range
 - Digital receiver requirements stress ADC fundamental limits

 

Ultra-Fast IC technology will have a major impact on Digital Receiver Technology

Linearity:

- Linearity of multibit quantizer determined by accuracy of voltage thresholds (process uniformity)
- 1 - Bit quantizer (= Comparator)
 - Inherently linear
- 1-Bit quantizer increases quantization noise



Resolution:

Oversampling (= Averaging)

- Improves Resolution @ 3 dB / Octave
- Requires High Speed Technology

Very High Oversampling Required for Practical Applications

 
 
- 10 bit, 50 MHz Requires Comparator Clocked @ 12.5 THz !!





Practical Realization : Add loop filter to shape noise and improve performance.

Bandpass DS Noise Shaping for Digital Receiver Applications



Conventional Oversampling ADC

  

Delta-Sigma Oversampling ADC

  

Bandpass Delta-Sigma ADC

  


The Noise Suppression Region Can Be “Tuned” Away From DC By Replacing The Lowpass Filter With A Bandpass Filter

Joe Jensen
(310) 317-5250
jfjensen@hrl.com

slide #5

Principle of bandpass DS modulation

 

$\Delta\Sigma$ modulator

Digitized output

- **A/D converter is put inside a feedback loop**
- **Quantizer error is reduced by the gain of the feedback loop**

Advantages: Unmatched resolution for high-IF digitization

Disadvantages: The DAC and input resonator still require full dynamic range of final desired output

- **Clock rate**
 - **SC DT DSM** maximum clock rate is limited by op amp bandwidth
 - maximum clock rate $\sim f_T/100$
 - **CT DSM** relax the restriction on op amp bandwidth
 - maximum clock rate $\sim f_T/20$
- **Switching Transients**
 - **SC DT DSM** have larger switching transients than **CT DSM**
- **Aliasing**
 - **SC DT DSM** require separate filter at their inputs to attenuate aliases sufficiently
 - **CT DSM** have free anti-aliasing
 - antialiasing is an inherent property of the mathematics of **CT DSM**

Available Devices in High Speed Bipolar Technology

- NPN transistors
- Resistors: Thin Film 50W /sq, Base Epi 800 W/sq
- Capacitors: Metal-Insulator-Metal


Consequences

- Low OpAmp Voltage Gain (typ < 100)
- No Simple Positive Current Sources or Active Loads
- No Switched Capacitors

Design Approach

- Continuous Time Integrators
- Transimpedance Amplifiers
- Fully Differential Circuitry to Minimize Noise Coupling
- Current-Mode Logic Minimizes Switching Noise

1st Order Low Pass DS Modulator

 



Basic Approach: High impedance current drive in a feedback integrator

- Tolerant of low amplifier gain
- Low voltage swing at input to integrating capacitors minimizes integrator leakage
- Allows current-summing for dac summing node
- Requires positive bias current source


Input transconductance cell outside feedback loop-determines overall circuit linearity

Transconductance Cell Saturation Characteristic

  
Converts differential input voltage to a differential current signal
Over all ADC linearity and distortion determined by the performance of this circuit



Integrator Design


 


 - **Differential amplifier with gain, A and feedback capacitors, C**
- **Low frequency gain determines the noise floor of DS modulator near DC**
- **Low frequency gain limited by ARC, where R is the effective resistance as seen at the current summing node**




Positive Current Source

  Positive current source needs to supply the current for the Gm cell and DAC
 The effective resistance of the positive current source determines the overall transimpedance gain (ARC)




G.A. De Veirman, et.al. JSSC Vol 27, No. 3, March 1992, pp 324-331

Comparator and DAC Cells

 



Asymmetric Rise and Fall Times

 Asymmetric Rise and Fall Times Produce a Signal Dependent Distortion



- **Ideal DAC waveform: average value of alternating sequence is zero**
- **Equal nonzero rise and fall times: average value of an alternating sequence is zero**
- **Asymmetric rise and fall times: alternating single pulses dc value not equal to zero**
- **Asymmetric rise and fall: alternating pairs of pulses has dc value different from alternating single pulses**


Symmetric Rise and Fall Times

  

- Symmetric finite rise and fall times do not effect the integrated area of the pulse train


- Balanced differential signals are inherently symmetric even if the individual components are asymmetric

Block Diagram

 


3.2 GHz Sample Rate

9525-01-013

 


DS Output Spectrum (0 to 1.5 GHz)

Die Photo

 

2nd Order DS Modulator
2.0 mm x 1.5 mm Die Size
250 HBTs

9525-01-014

 

Signal Band for 100 MSPS ADC



↑
SFDR=
70 dB
↓

Joe Jensen
(310) 317-5250
jjensen@hrl.com



slide #17

Conversion of Low Pass DS Modulator to Bandpass DS Modulator

Low Pass

  


Bandpass

  


Resonator Sensitivity to Interconnect Delay - Q-Tuning Circuit

 
Lead-lag network required for 180° phase.



 
Frequency and Q can both be tuned by varying a gm



 
Resonator response is sensitive to R_i . Need tunability



Redraw resonator

 


 Equivalent circuits if: $gm_i = gm_1 gm_2 R_i$




4th Order Bandpass DS Modulator Continuous Time Architecture

Feedback DS Modulator

 

Qfb reduces signal delay

 - Improves stability
- Improves wideband SNR
- Improves gain flatness



Q-tuning eliminates need for positive current source





- Q feedback cancels finite impedance of pull up resistors

InP HBT IF Bandpass DS Modulator


4th Order, 1-Bit DS, 4 GSPS, 2nd IF Sampling

* Published JSSC Oct. 2004

Conventional Analog I/Q Receiver

   
 


 4th order, tunable IF, bandpass DS Modulator




Enhanced Performance
Lower Power
Lower Size & Weight
Lower Cost

IF Sampling Receiver

  

Active GM-C 4th Order

 


Advantages

- Small size for lower frequencies
- Electronically Tunable

Disadvantages

- Higher noise figure
- Low Linearity
- Higher Power Dissipation
- Frequency range limited to $< f_T/20$

Passive L-C 4th Order

 


Advantages

- Lower Noise Figure
- High Linearity
- Higher Frequency Operation
- Lower Power

Disadvantages

- Harder to electronically tune
- Large size for low frequencies < 500 MHz

Multi-bit DS Modulators

 

Advantages


- High resolution over wider bandwidth
- Increased stability for high order DS modulators
- Reduced sensitivity to DAC timing errors

Disadvantage



- Resolution limited by multi-bit DACs element mismatch and linearity

InP HBT 1st IF Bandpass DS 4th Order, 3-Bit, 4GSPS, 1.4GHz IF Sampling


* Published CICC 2003

 


Resonators and G_m -cells

  

 Q-tuned internal LC resonators ($Q \sim 10$)
No mismatch shaper




Multibit DAC Mismatch Errors


 


DAC Mismatch Shaping

 - Moves DAC mismatch errors away from signal
- Eliminates spurs caused by DAC mismatches
- Enables high resolution signal generation using a multi-bit DAC





3-bit pipelined mismatch-shaped DAC

  


3-bit, 2 GS/s DS DAC with Tunable Mismatch Shaper


*Published ISSCC 2004

  

Single-tone

 

 10-20 dB improvement in SNR and IMD from mismatch shaping
SNR > 68 dB/1 MHz BW from 250-750 MHz IF
IMD < -80 dBc from 250-750 MHz IF



- **Bandpass DS modulation is an ideal ADC architecture for digital receivers**
 - **Elimination of downconversion stages and analog IF filters**
 - **Improved I and Q matching**
 - **Improved performance with digital modulation schemes**
 - **Improved flexibility with communication standards**
 - **Reduction of size, weight, power, and cost for multimode receivers**